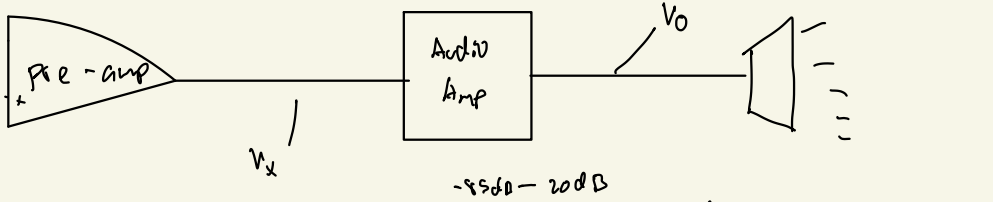


Goal:

Aiming for 100-200mW RMS (8+) of audio at speakers

Sum of radio/Alarm signal



$$P = IV$$

$$P = \frac{V_{rms}^2}{R}$$

$$V_{rms} = \sqrt{PR}$$

$$= \sqrt{(200 \cdot 10^{-3} \text{ W})(8 \Omega)}$$

$$V_0 = (1.26 \text{ V})(2\sqrt{2}) = 3.56 \text{ V peak-peak}$$

Configuration:

SE/BTL → drive 1

20dB

$$\text{dB} = 20 \log_{10} \left[\frac{V_0}{V_{in}} \right] - \text{Voltage/Gain ratio}$$

$$\frac{\text{dB}}{20} = \log_{10} \left[\frac{V_0}{V_{in}} \right]$$

$$10 \frac{\text{dB}}{20} = \frac{V_0}{V_{in}}$$


$$V_{in} = \frac{V_0}{10^{\frac{\text{dB}}{20}}} \quad \text{dB} = 20$$

$$V_{in} = \frac{3.56 \text{ V}}{10^{\frac{20}{20}}} = 0.356 \text{ V}$$

$$V_k = 356 \text{ mV}$$

peak-peak

Calculations

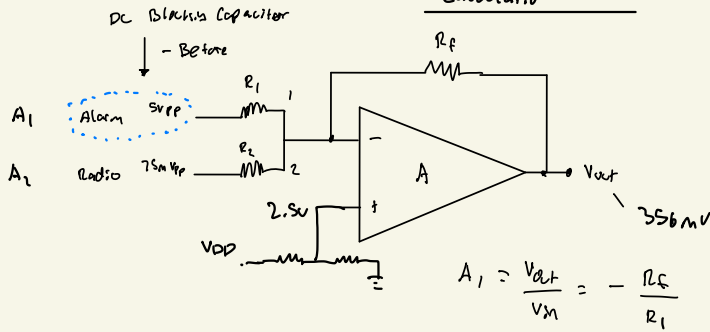

Based on kit:

$$R_f = 220\Omega$$

Choose 220Ω for R_f

Need to have 2.5V at

positive of the Amplifier to

keep the signal at 2.5V

so it does not clip.

$$\frac{.356}{5V} = \frac{R_f}{R_1}$$

$$.07152 = \frac{R_f}{R_1}$$

$$R_1 = \frac{220}{.07152} = 3.1k\Omega$$

$$A_2 = \frac{V_{out}}{V_{in}} = \frac{.356V}{.075V_{pp}} = 4.74$$


$$A_2 = \frac{-R_f}{R_2}$$

$$R_2 = \frac{220}{A_2}$$

$$R_2 = 46.34\Omega$$

input capacitor - high pass

$$C_i = \frac{1}{2\pi R_i f}$$

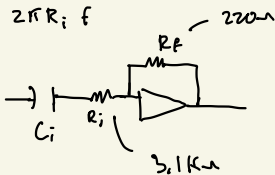

Lowest musical note is 16.32Hz

We want to be able to account for all musical notes.


The kit has 4.7μF capacitor

$$C = 4.7\mu F$$

$$f_c = \frac{1}{2\pi R_c} = \frac{1}{2\pi (3.1k\Omega) (4.7\mu F)} \approx 11Hz$$

Anything below 11Hz will not go through the high pass filter. We want to block DC voltage so after pre-amp output does not get saturated.

Volume - P Wm Calculation

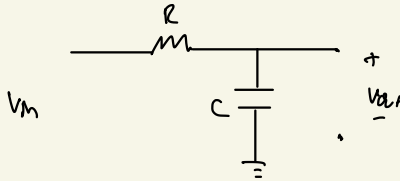

$$X_C = \frac{1}{2\pi f C}$$


$$C = .1 \mu F$$

$$V_{out} = V_{in} \frac{X_C}{\sqrt{R^2 + X_C^2}}$$


Based on kit choice: $R = 1k\Omega$ $C = .1\mu F$

$$f_c = \frac{1}{2\pi R C} = \frac{1}{2\pi (1k\Omega)(.1\mu F)} \approx 1591 \text{ Hz}$$

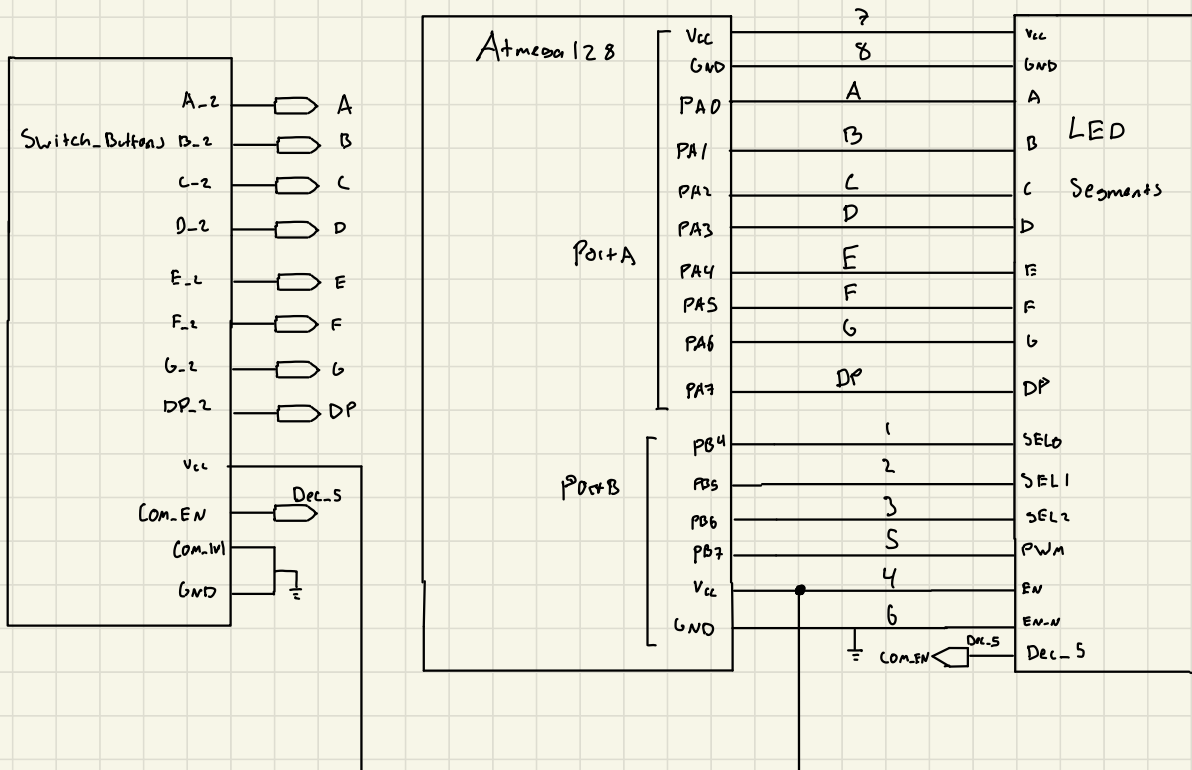
We don't want to low of a cut off frequency
or it'll take a long time for the output voltage
to reach the desired DAC voltage.





Name	Benson Ton
Date	10/30/2021
Title	Top Level

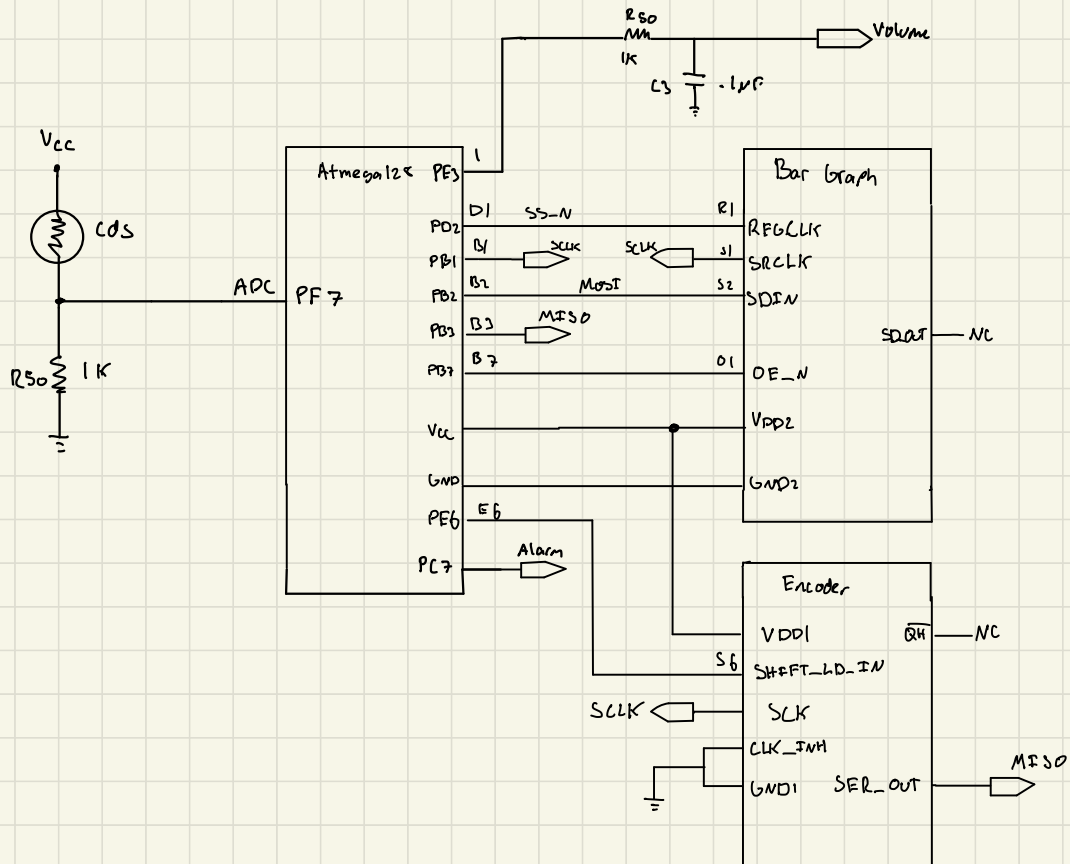


Name	Benson Ton
Date	11/16/2021
Title	Top level with Bar graph, encoder, cds cell

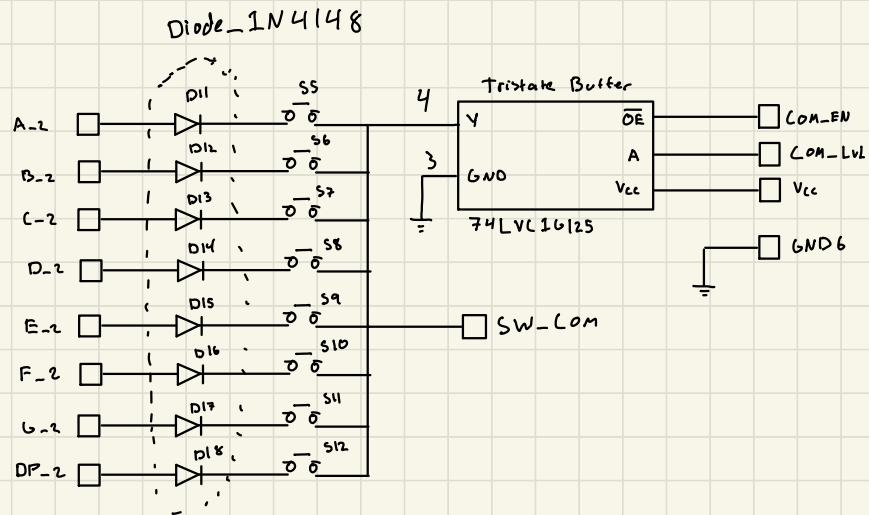


Name	Benson Ton
Date	10/10/2021
Title	Switch Board

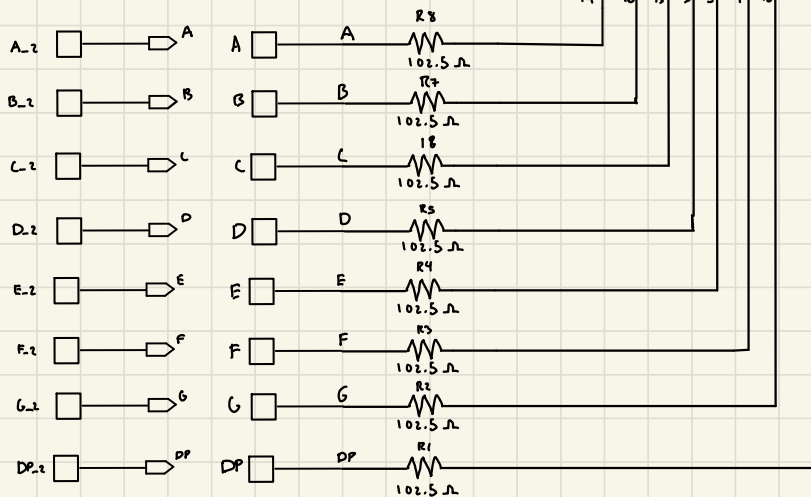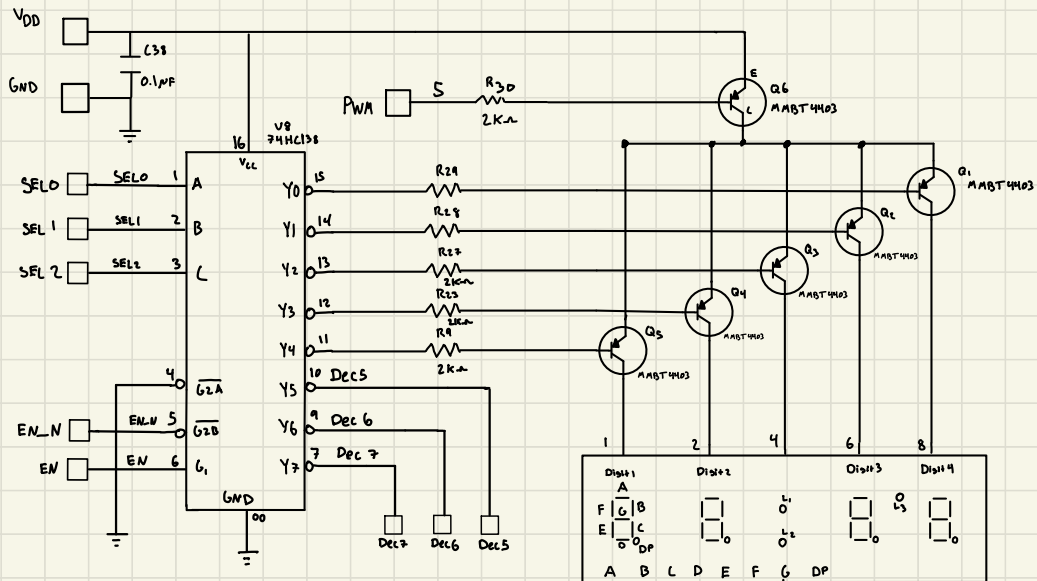


Name	Benson Ton
Date	10/10/2021
Title	Segments

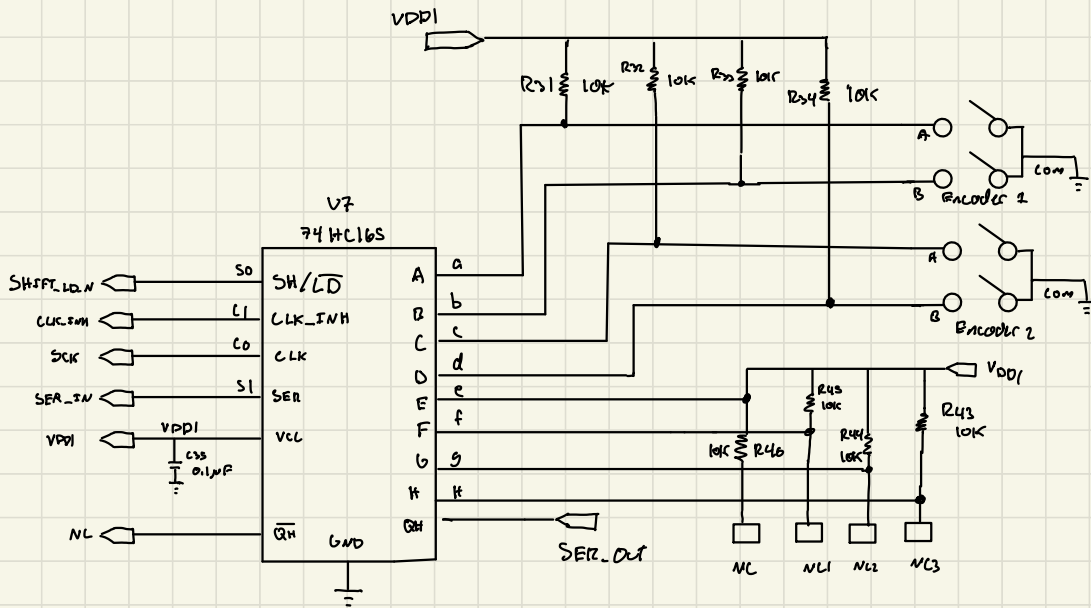

Name	Benson Ton
Date	10/30/2021
Title	Encoders

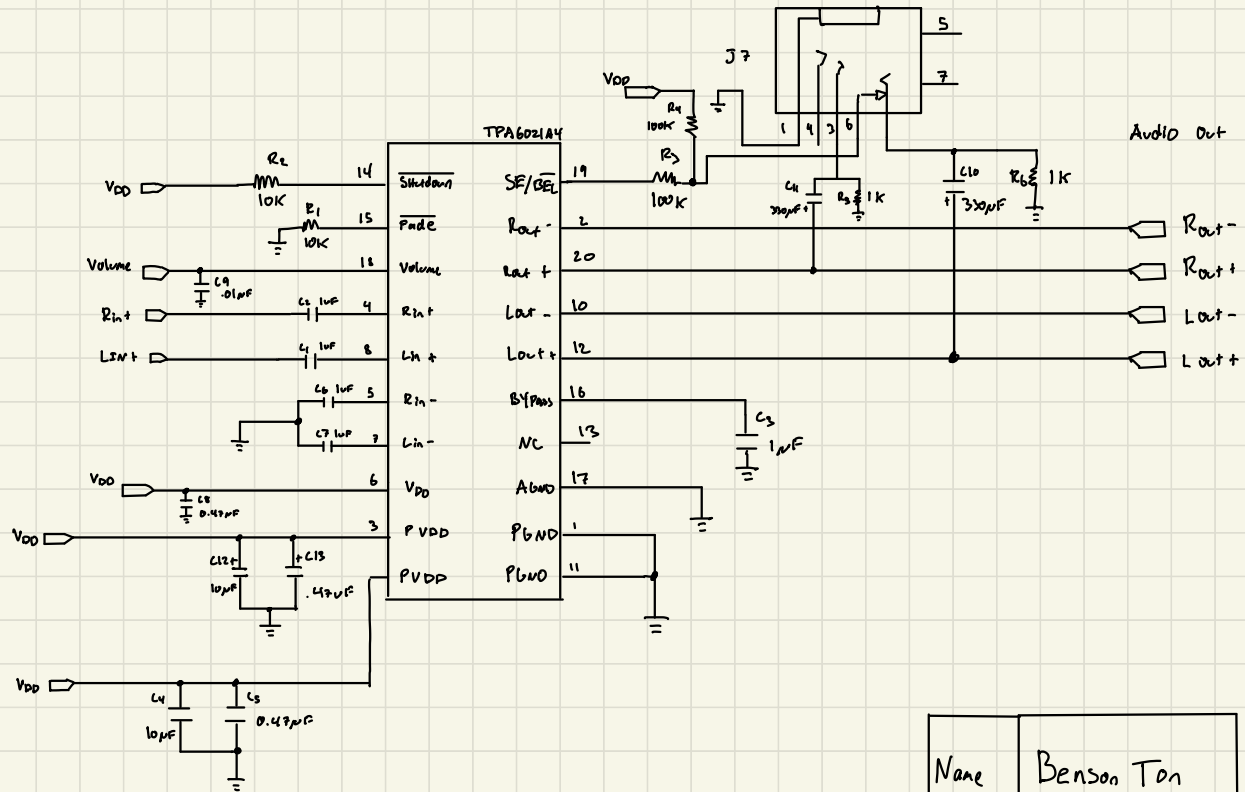

Name	Benson Ton
Date	11/16/2021
Title	Audio Amp

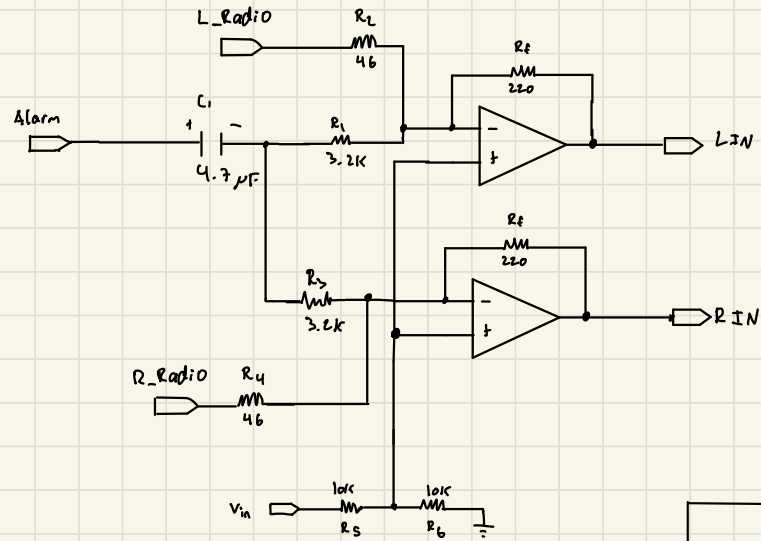

Name	Benson Ton
Date	11/14/2021
Title	Pre-OP-amp